

# TASK 8: GATE QUESTION SOLUTION

KHUSHI THAKUR


## Contents

<b>1</b>	<b>Problem</b>	<b>2</b>
<b>2</b>	<b>Introduction</b>	<b>2</b>
<b>3</b>	<b>Components</b>	<b>2</b>
<b>4</b>	<b>Solution</b>	<b>3</b>
4.1	Karnaugh Map . . . . .	3
4.2	Truth Table . . . . .	3
<b>5</b>	<b>Connections</b>	<b>4</b>
5.1	LED to Arduino . . . . .	4
5.2	Input Pins to Arduino . . . . .	4
5.3	Setting Input Pin Values . . . . .	4
5.4	Repository . . . . .	4

## 1 Problem

(GATE CS Q26- YEAR 2002)

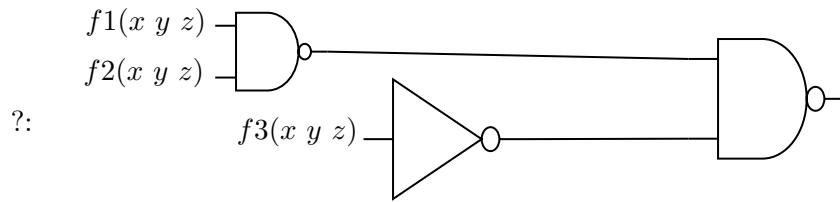**Q.26** Consider the following logic circuit where inputs are functions  $f_1, f_2, f_3$  and output is



## 2 Introduction

For a given set of Boolean Logic Inputs, we can define the following terms:

- **Minterm** is a boolean expression resulting in an output of 1 for the minimum number of cells in a Karnaugh-Map (K-Map) and 0 in other cells.
- **Sum of Products** is a boolean expression for the *Sum* (OR) of various *Product* (AND) terms.
- **'do not care'** terms for a boolean expression are the set of input values for which the output of the function does not matter. The value for these can be taken as 0 or 1 by choice

## 3 Components

Component	Value	Quantity
Arduino	UNO	1
Breadboard	-	1
LED	-	1
Jumper Wires	M-M	10
Resistor	220 $\Omega$	1

Table 1: Table of Components

## 4 Solution

### 4.1 Karnaugh Map

		AB			
		00	01	11	10
C	0	0	0	0	0
	1	0	0	0	1

The final expression is of output is  $Y = F(x,y,!z)$

Logic for the code will be  $Y = X \& \& Y \& \& !Z$

### 4.2 Truth Table

X	Y	Z	F(OUTPUT)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

## 5 Connections

### 5.1 LED to Arduino

LED connections to Arduino are as follows:

Arduino	D2	GND
LED	+	-

Table 2: LED Connections

### 5.2 Input Pins to Arduino

Input Pin Connections to Arduino are as follows:

Arduino	D6	D7	D8	D2
Term	X	Y	Z	F

Table 3: Input Pin Connections

### 5.3 Setting Input Pin Values

The values of the Input pins are taken by connecting them to either 5V or GND according to Truth Table

### 5.4 Repository

Code is online at the following repository:

<https://github.com/KhusheyT/blob/main/codes/codes.ino>